



# Minecraft ALU Module

By: Brandon Esebag, Maria Aponte, Aaron Hoang, Jonathan Liu

# What is Minecraft?



- Minecraft is a kid's game released in 2009
- The game is an open world sandbox where the player can essentially do anything
- As per the name Minecraft, there is an emphasis on **mining** ores and **crafting** tools
- The world is voxel based and procedurally generated


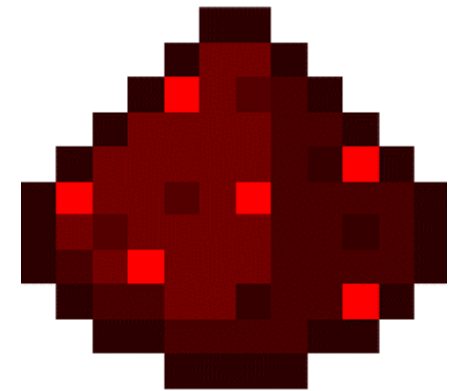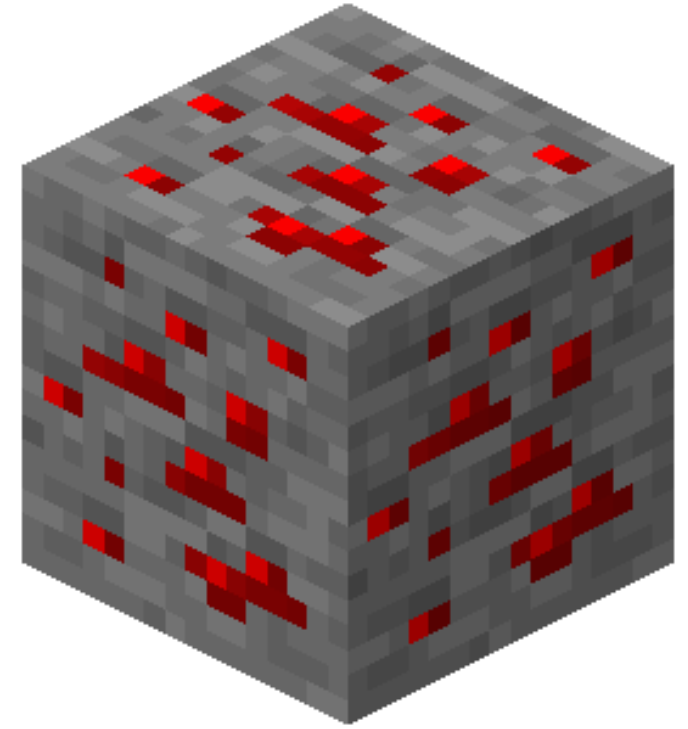
# What is Redstone?



---

- Most ores in Minecraft (eg Diamond, Gold, Iron, etc) are real materials...
  - Redstone is a fictional ore that enables specific game mechanics!
- Redstone is an in-game resource that behaves as a conductor
- In combination with other items in the game (levers, repeaters, pistons, etc.) someone can use redstone to create primitive electronics in the game
- Normal redstone uses include:
  - Controlling doors
  - Controlling mine-carts
  - Using pistons to control water/lava flow


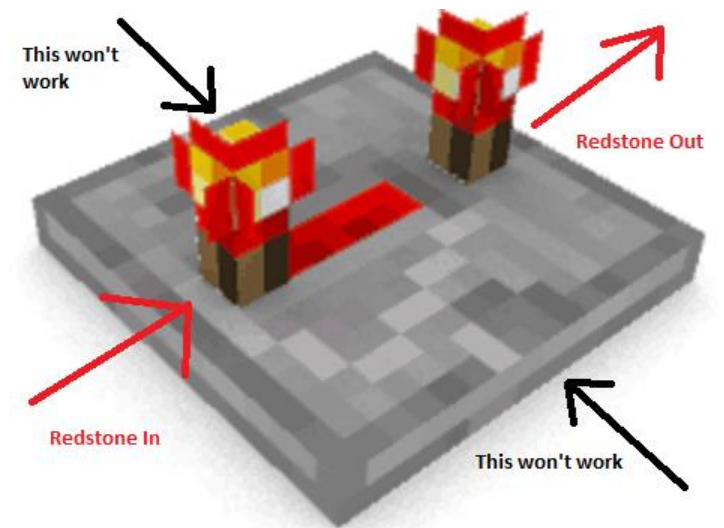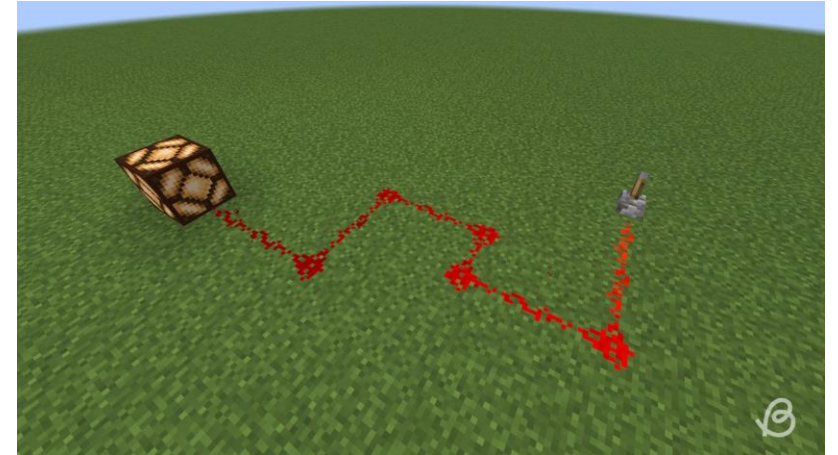
# Redstone Dust Placement

- Redstone dust can be placed to form wires as shown below (top)
- Redstone wire signals attenuate from value 15  $\rightarrow$  0 over 16 blocks of travel
- A redstone repeater (bottom) amplifies any signal  $> 0$  back to 15 with a time delay of 0.1 - 0.4 s







# Combinational Logic in Redstone

It is even possible to create combination circuits in the game with redstone


This leads us to what we want to do...

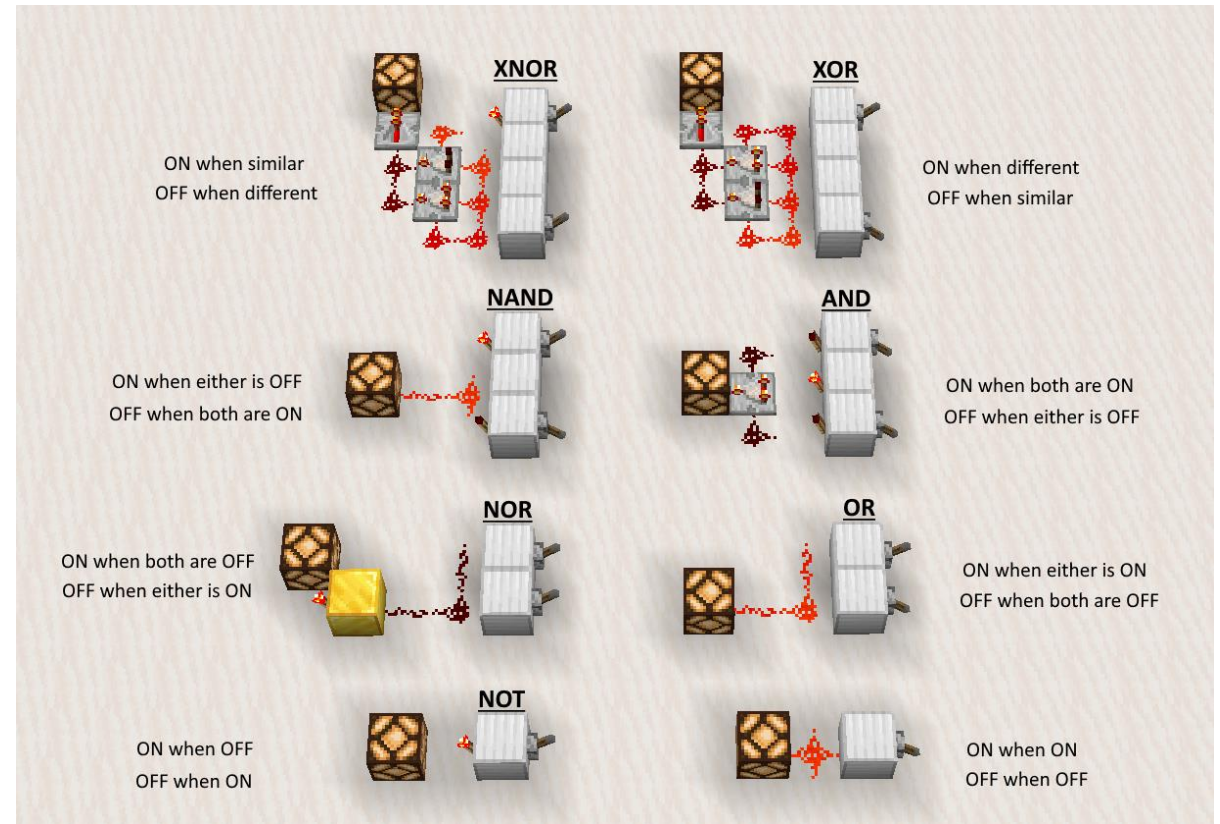


# 16 bit ALU Circuit Design

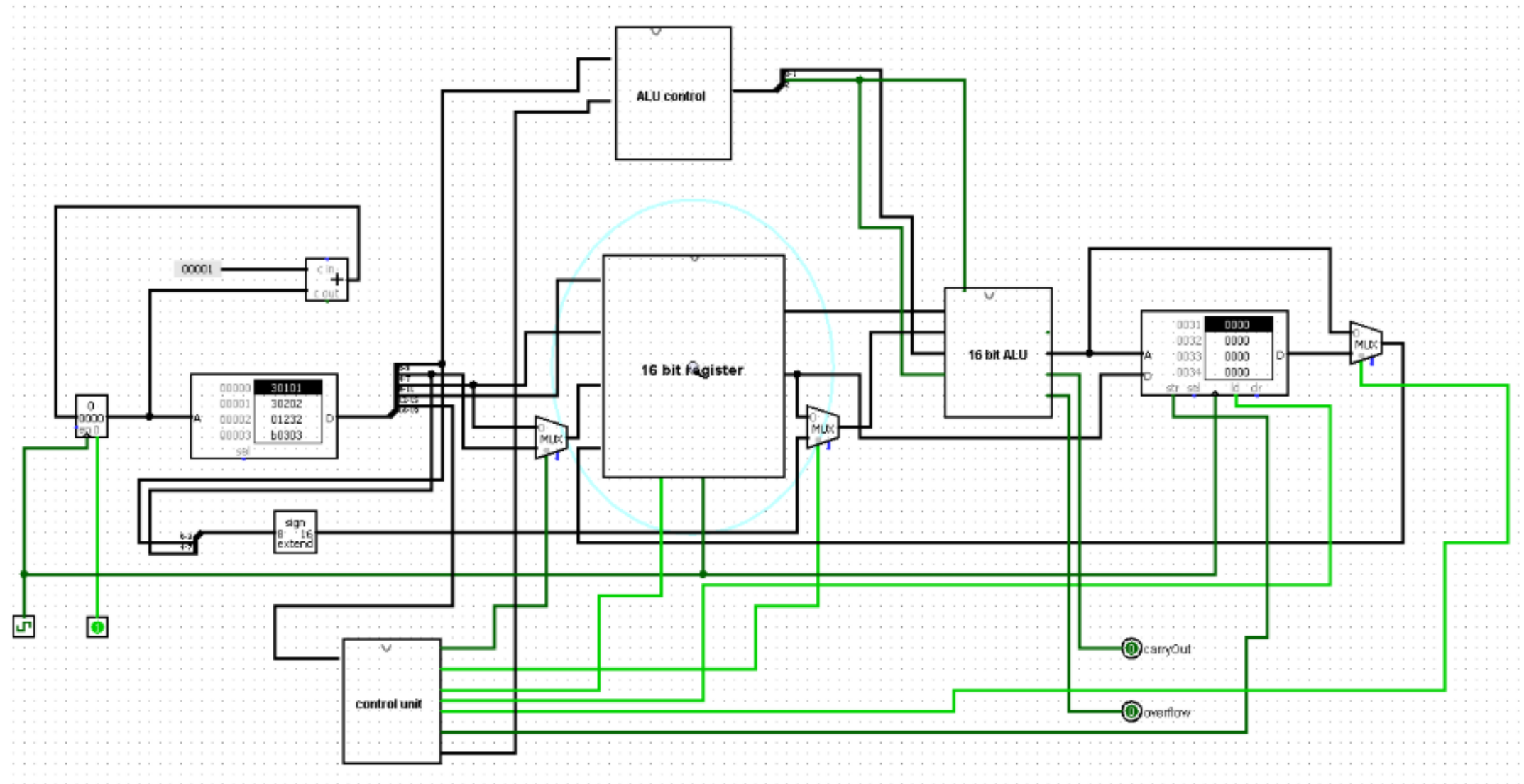

# Control Unit

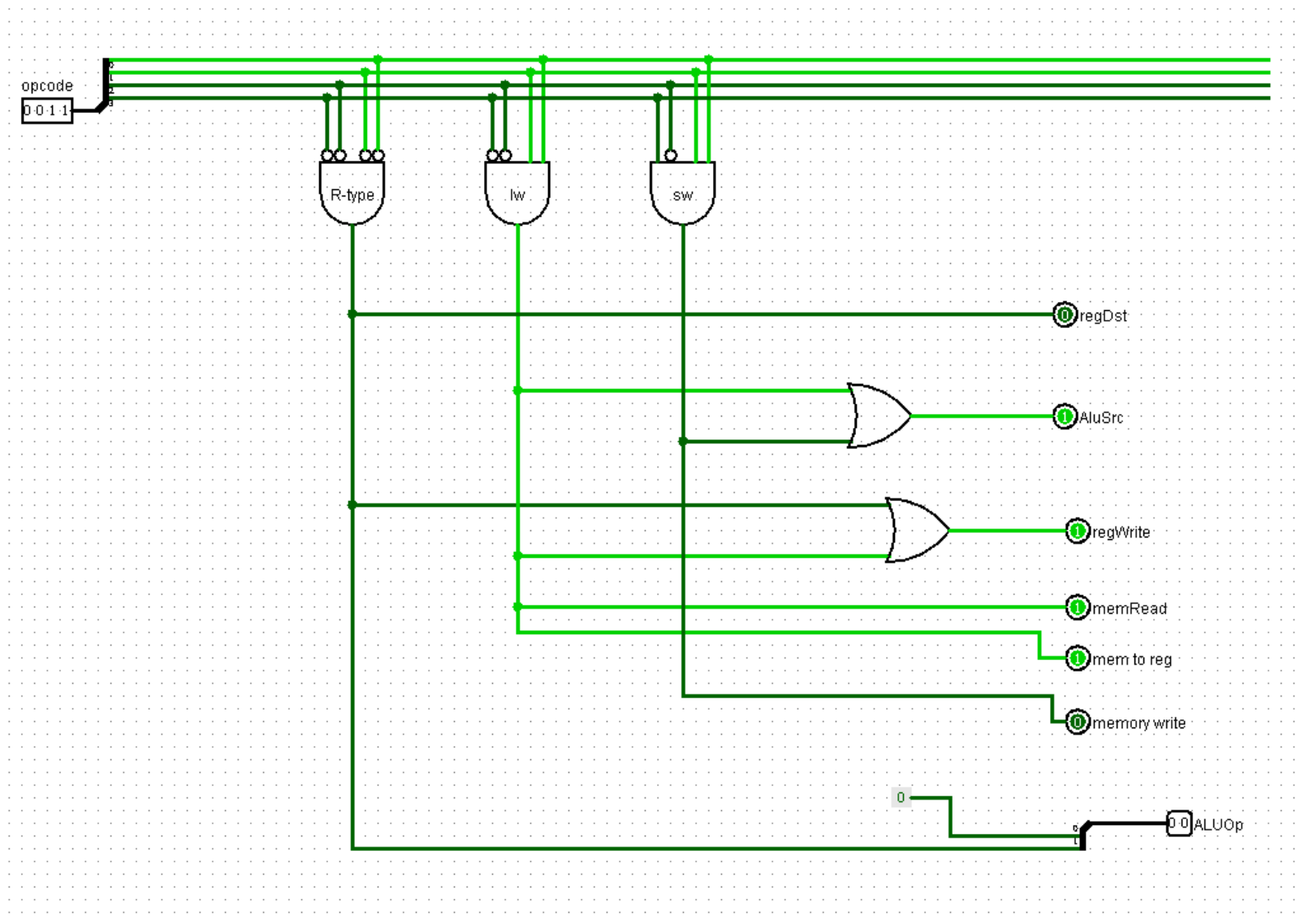



# ALU Control

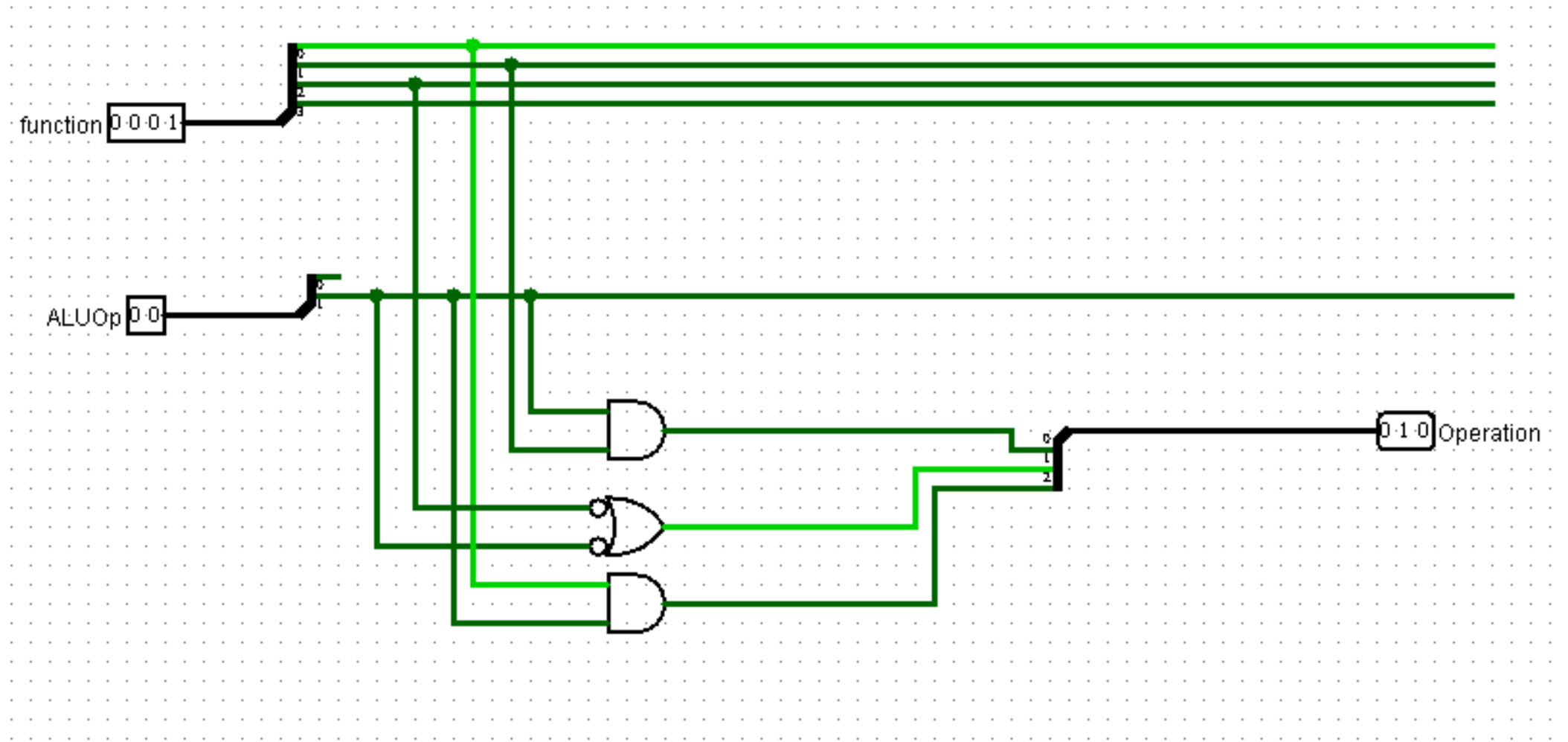



# 16-Bit ALU

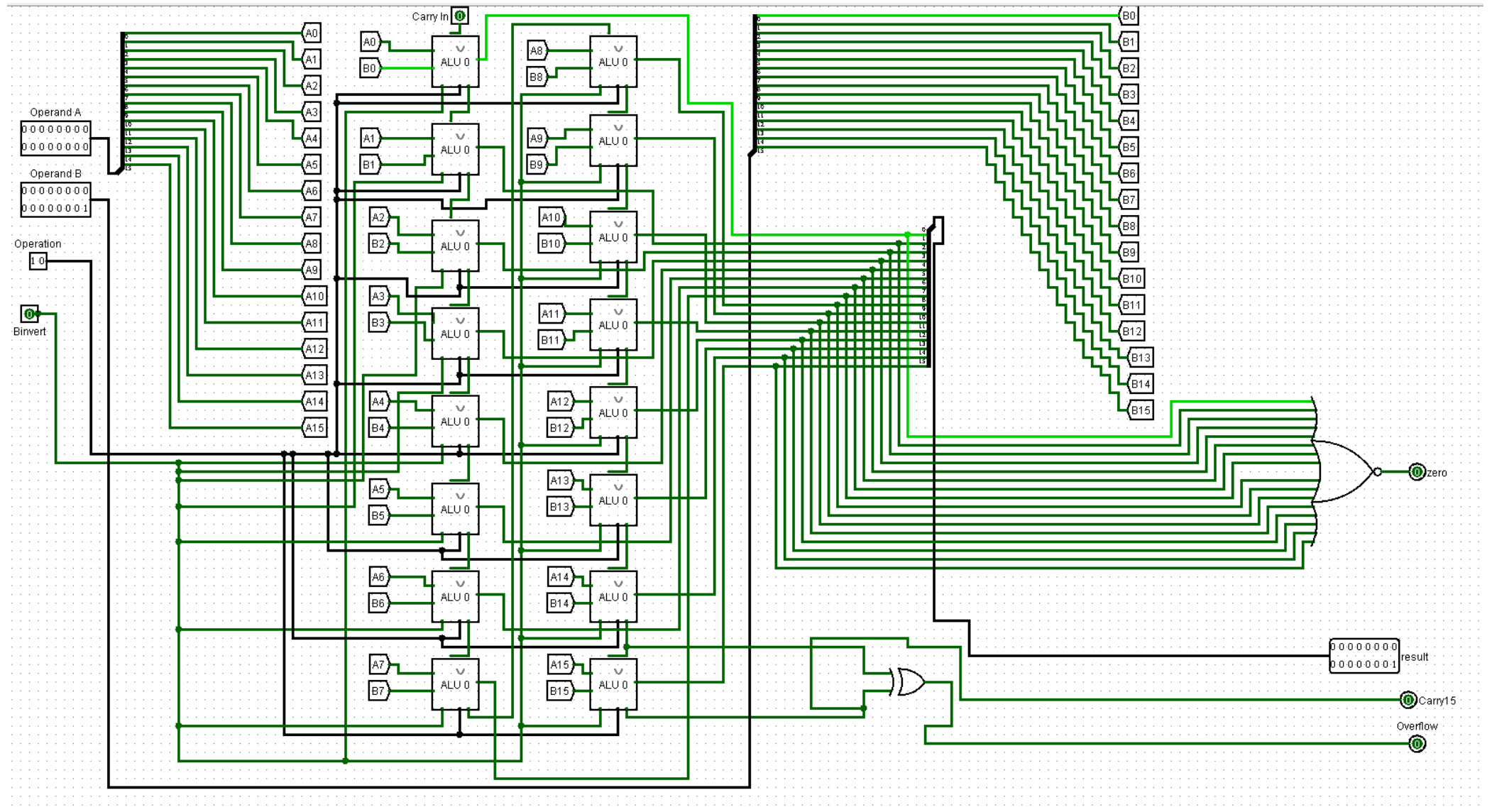

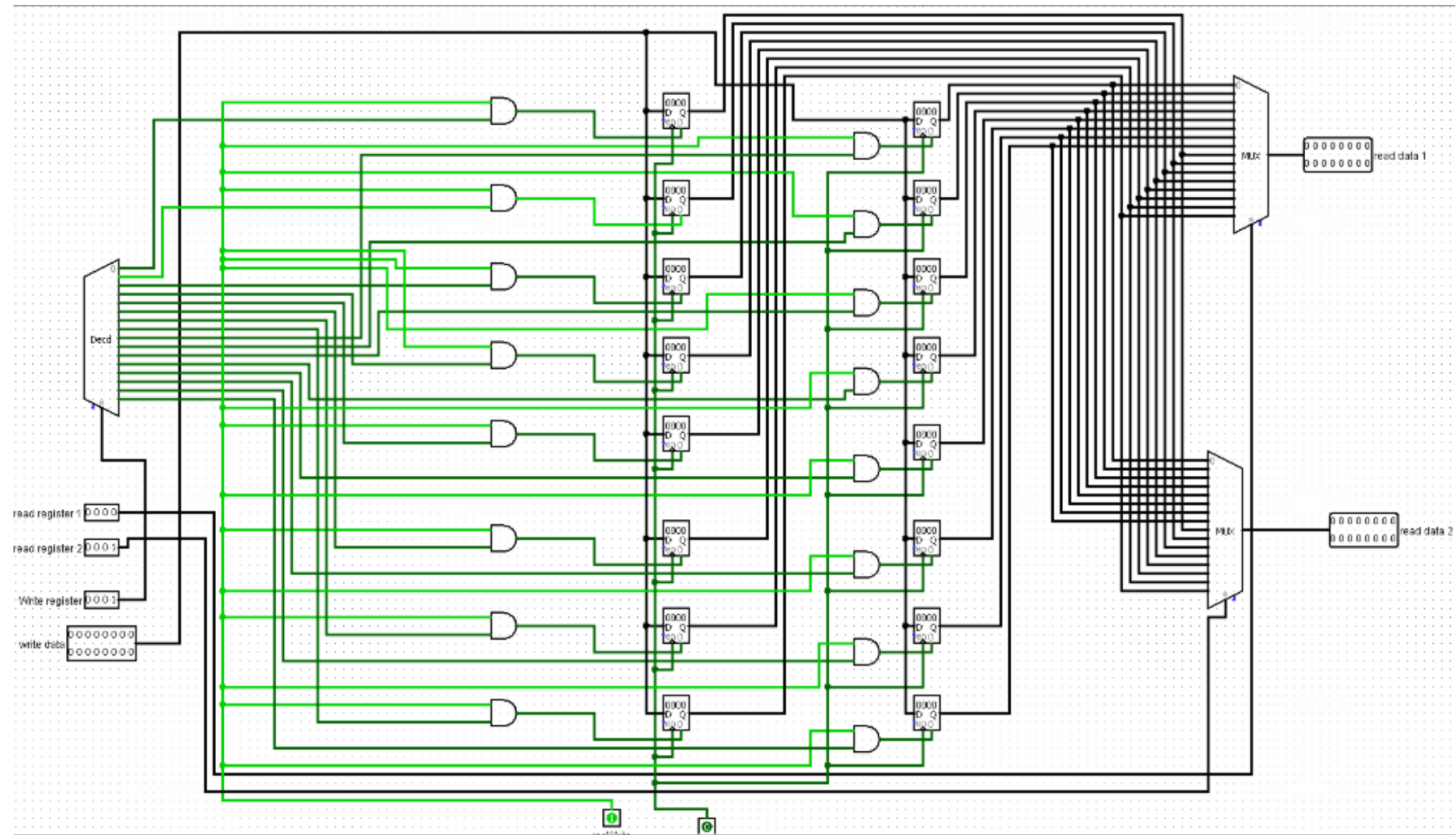

# Components Overview

- **1. 16-bit Register**

- Acts as a storage unit for intermediate or temporary data.
- Data from this register is sent to the ALU for computations.

- **2. 16-bit ALU**

- Performs arithmetic and logic operations such as addition, subtraction, AND, OR, and NOT.
- Accepts inputs from the 16-bit register and another source (multiplexer-controlled).
- Outputs the result of computations to either RAM or another component.

- **3. RAM (Data Memory)**

- Stores and retrieves data using the address generated by the ALU.
- Data input (D) is sourced from the ALU output, while data output is sent back to the system through another multiplexer.

- **4. Multiplexers (MUX)**

- Allow selection of data from multiple sources based on control signals.
- Control the flow of data between the ALU, RAM, and registers.

- **5. Immediate Values**

- The immediate values (from instruction encoding) are used as direct inputs for operations or memory addressing.
- Extended to 16 bits to align with the width of the system.

This project is a comprehensive implementation of a 16-bit Arithmetic Logic Unit (ALU) integrated with registers and RAM. It demonstrates the fundamental structure and functionality of a simple processor system, focusing on memory access and data manipulation through arithmetic and logic operations.

# Deliverables


- **Core Features**

- **Arithmetic Operations:** The ALU can add or subtract data from the register and other inputs.
- **Logic Operations:** Perform bitwise operations like AND, OR, and NOT.
- **Memory Access:** The ALU generates addresses for RAM to perform read/write operations.
- **Data Routing:** Multiplexers route the correct data to the required components based on control signals.

- **Example Operation**

- **Input Data:**
  - Data is loaded into the 16-bit register and RAM.
  - Immediate values are prepared (if needed).
- **ALU Computation:**
  - Register 1 sends its data to the ALU.
  - Register 2 provides data for a secondary ALU input via the multiplexer.
  - The ALU computes the result and outputs it.
- **Memory Write:**
  - ALU output serves as an address for RAM.
  - Data from Register 2 is written to the specified address in RAM.
- **Memory Read:**
  - ALU generates an address.
  - RAM sends the data stored at that address to the next stage (e.g., a register).

# Gantt Chart

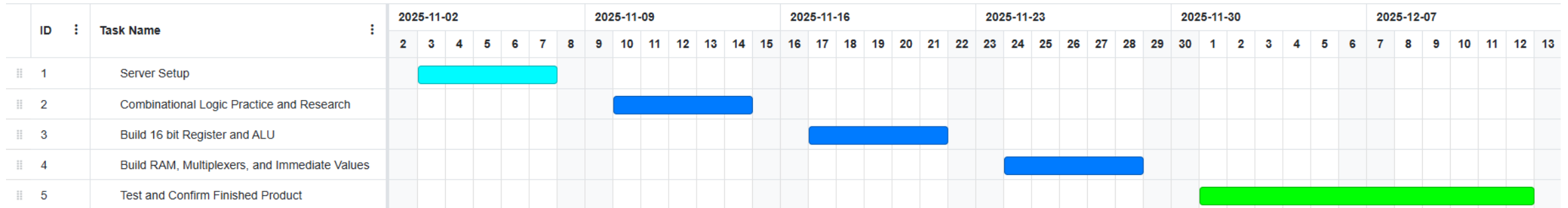

- Week One: Server Setup
- Week Two: Build and Test All Combinational Logic Elements Using Redstone
- Week Three: Build 16-bit Register and ALU
- Week Four: Build RAM, Multiplexers, and Immediate Values
- Week Five: Combine Together and Test Finished Product